

Measure Transistor Tracer Curves

- with Function Generators and Oscilloscope**

Sam Wright

1/22/2026


Function Generator: to stimulate and test circuits

It produces pre-defined electrical signals

- ▶ Common waveforms: sine, square, triangle
- ▶ Acts as a controllable voltage source


The front panel of a function generator in the lab

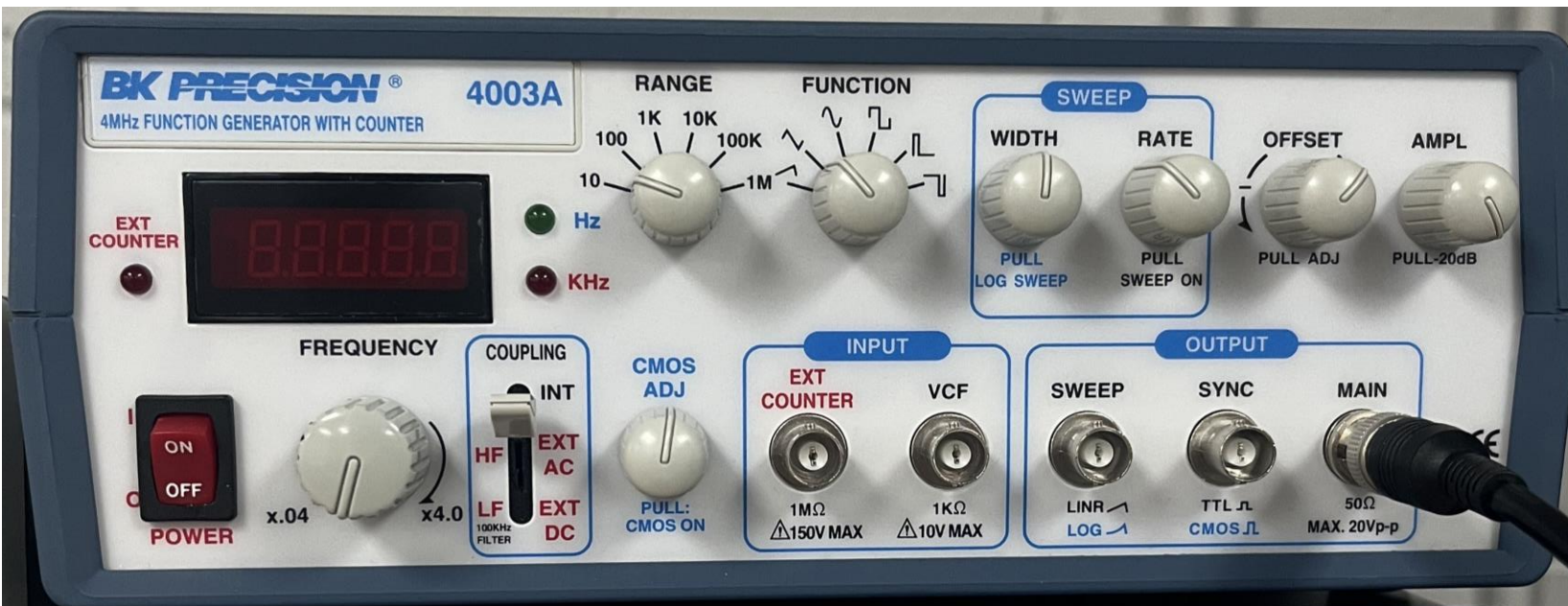We have function generators in different shape and sizes



Basic Steps of Function Generator Controls

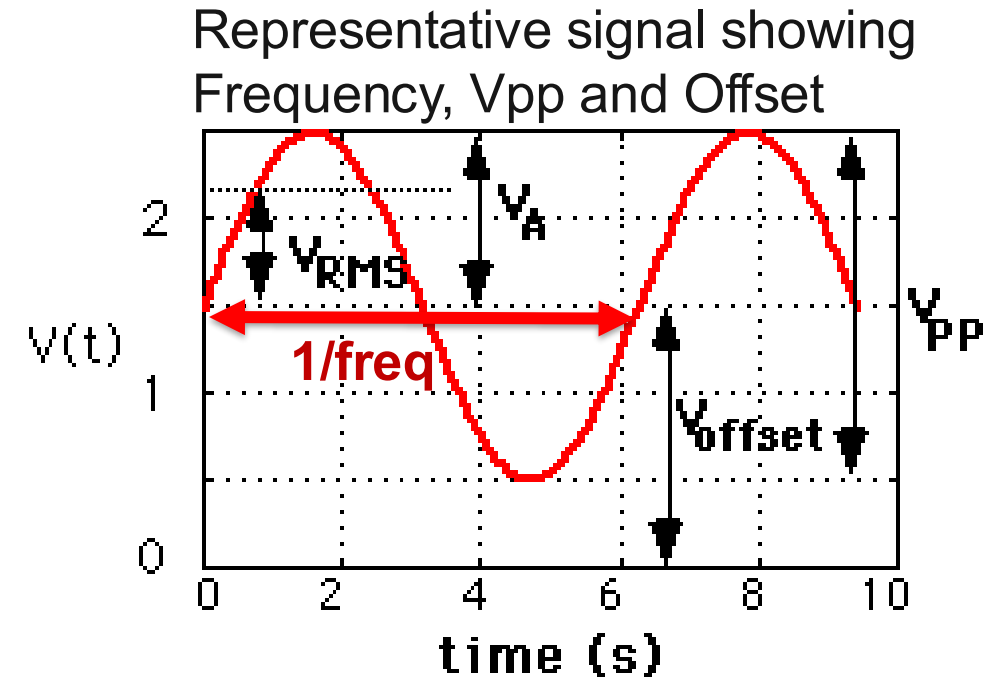The front panel of a function generator in the lab



<https://www.hit.bme.hu/>

Step 1: Power ON

Step 2: Chose the Waveform

Step 3: Adjust the output specs (you can do it live):

- ▶ Frequency controls how fast the signal repeats (Hz)
- ▶ Amplitude sets signal size (V_{pp})
- ▶ DC offset shifts the signal up or down


Oscilloscope: measures and display in real time

- Instrument that measures voltage versus time
 - ▶ Allows observation of waveform shape and timing
 - ▶ More informative than a multimeter for AC signals

We got many different scopes in the lab




You probe, you see signals

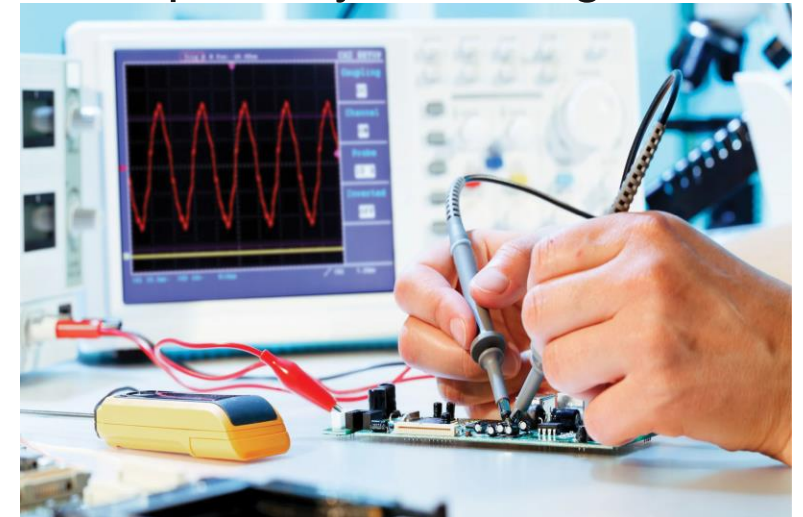

Oscilloscope Signal Basics


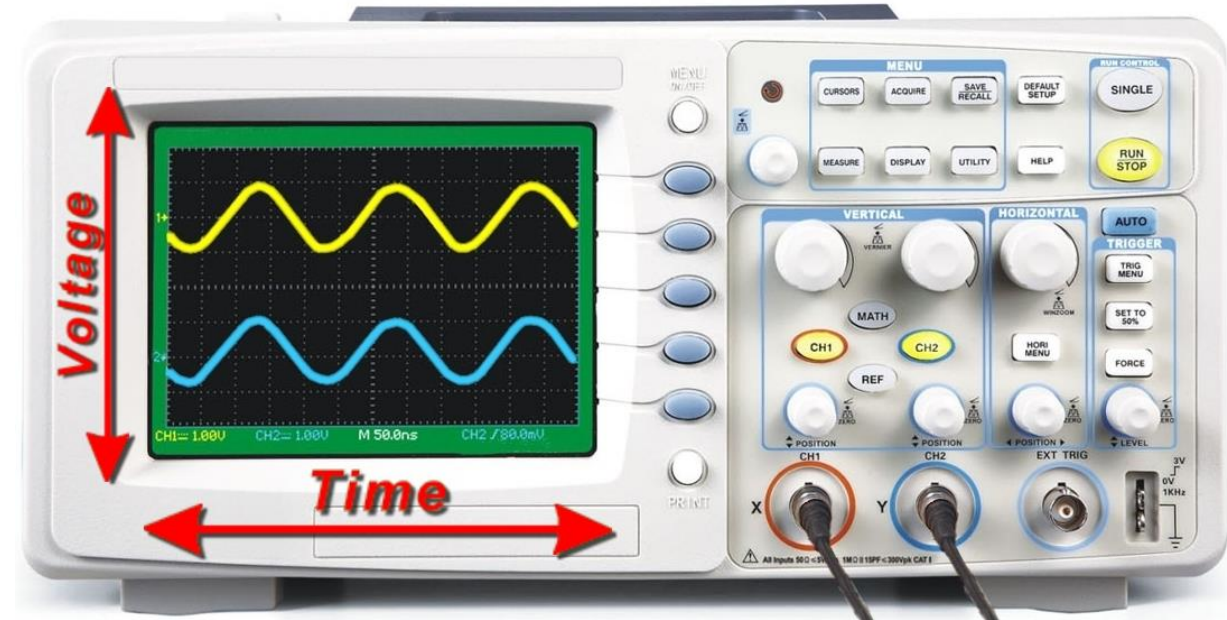
- Vertical axis represents voltage (V/div)
 - ▶ Horizontal axis represents time (s/div)
 - ▶ Each grid division is a unit of voltage or time
 - ▶ Multiple channels allow multiple inputs and signal comparison




X-Y Mode

- Removes time from the display
 - ▶ Channel 1 controls the X-axis
 - ▶ Channel 2 controls the Y-axis
 - ▶ Used to plot one voltage versus another

Time series

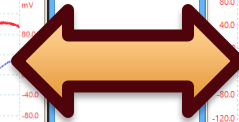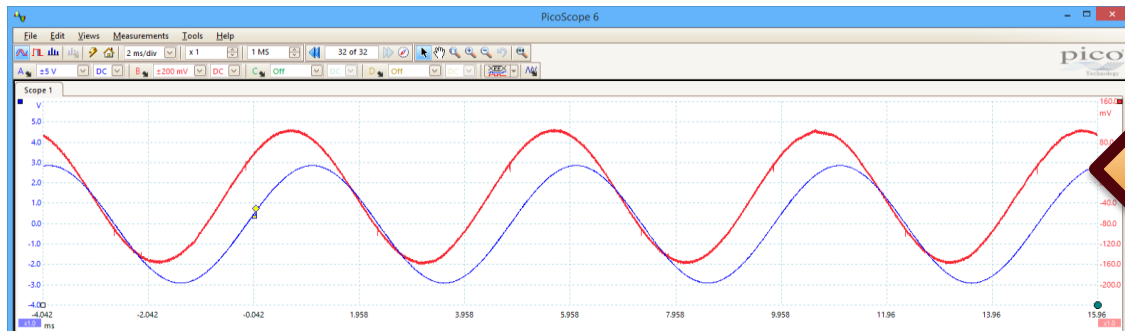

X-Y mode

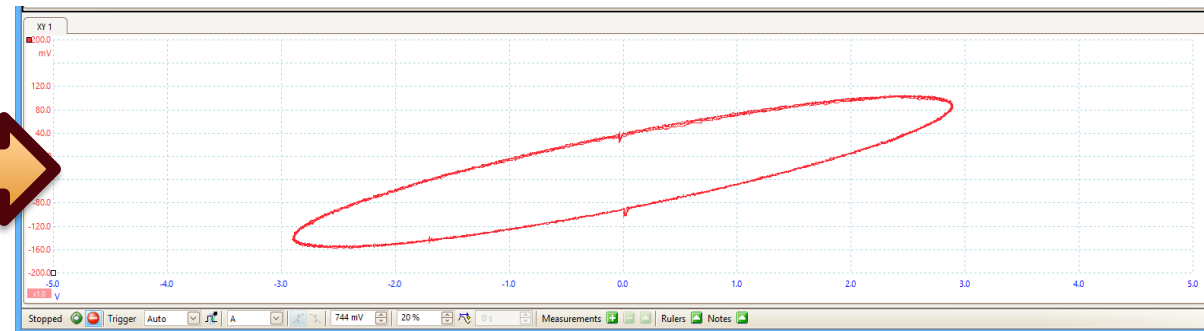

Transistor and Transistor Tracer Curves

- Plot of collector current (I_c) versus collector-emitter voltage (V_{cb})
 - ▶ Each curve represents a different base current
 - ▶ Shows cutoff, active, and saturation regions
 - ▶ Provides visual understanding of transistor operation


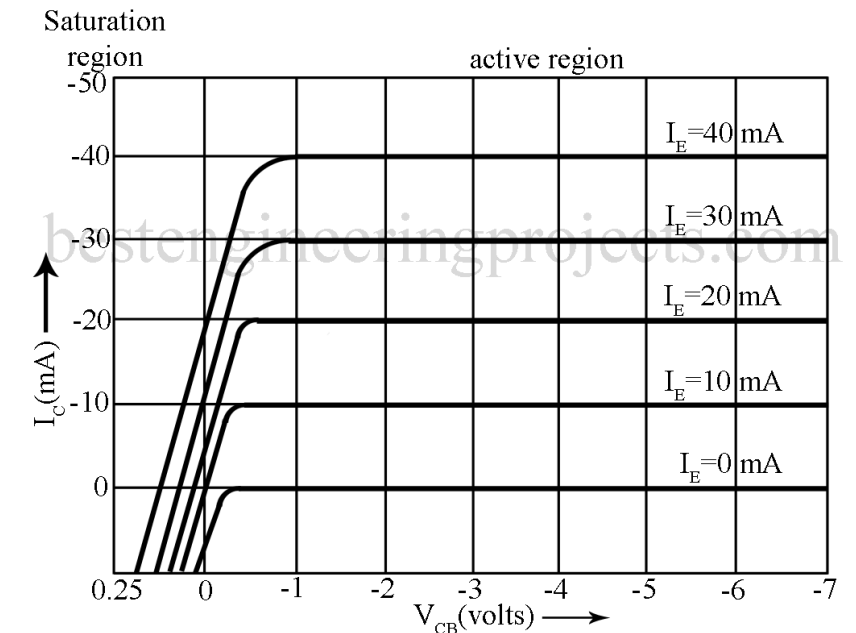
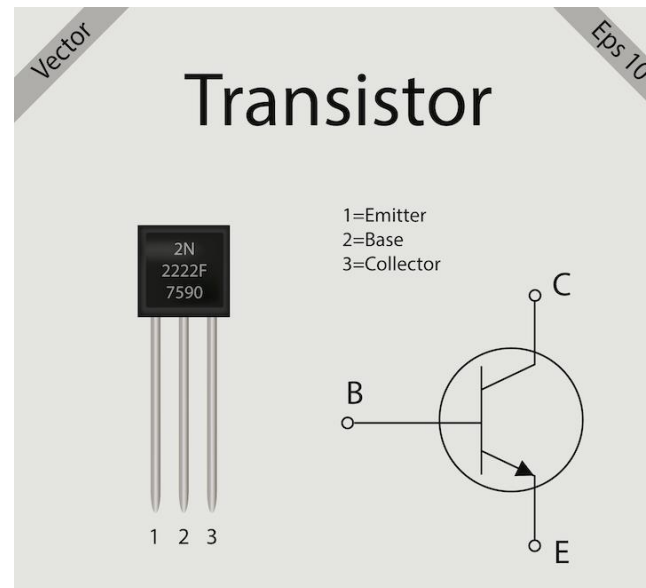
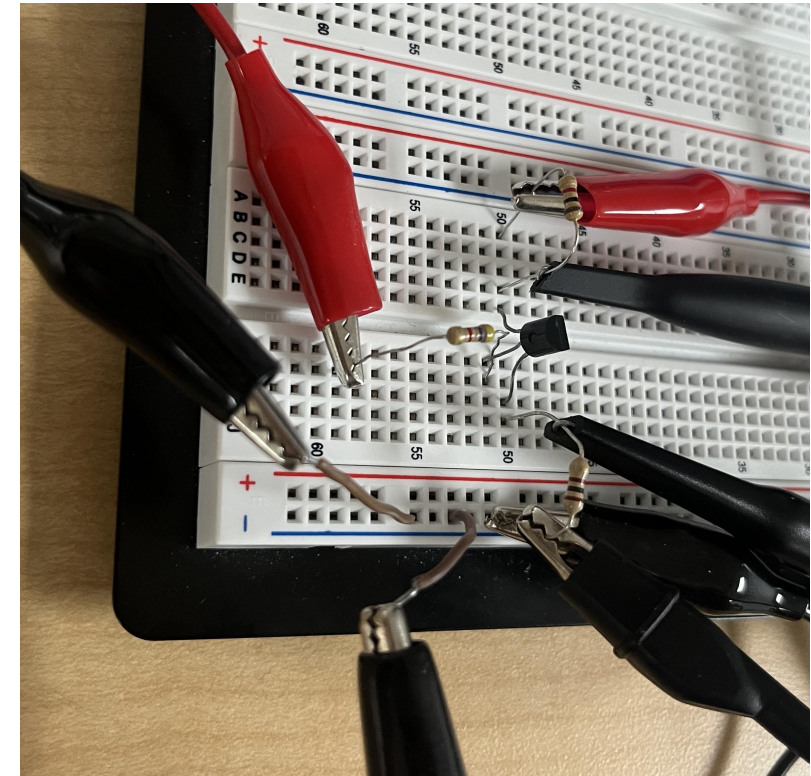


Figure 3: Static Output Characteristics of a typical PNP Ge grown junction transistor in CB configuration

Curve Tracer Circuit Setup

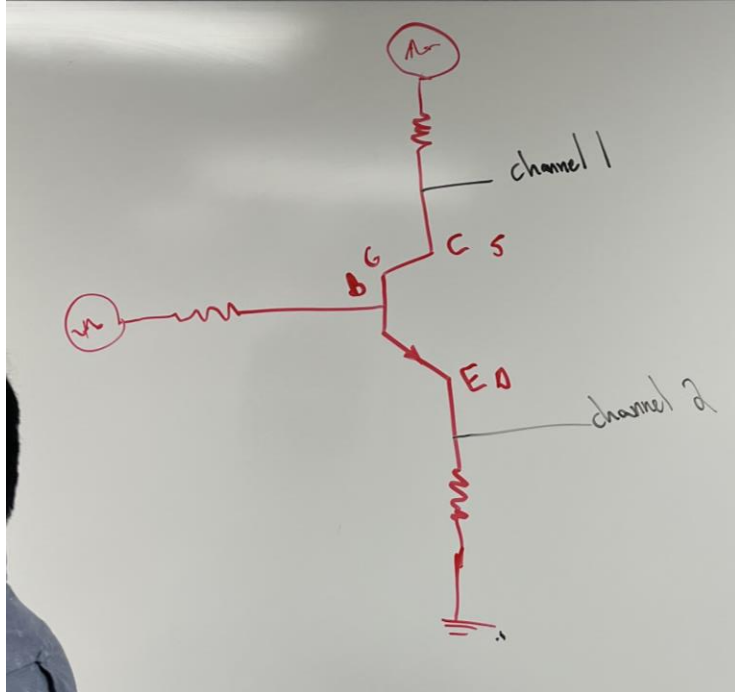- Function generator sweeps collector voltage with a triangle wave
 - ▶ Base current set using a resistor and triangle wave
 - ▶ Sense resistor converts current to voltage
 - ▶ Oscilloscope in X-Y mode displays I_c vs V_{ce}



Results and Observations

- Multiple curves visible simultaneously on the oscilloscope
 - ▶ Flat regions indicate active transistor operation
 - ▶ Knee region shows saturation behavior
 - ▶ Curve spacing relates to transistor gain (β)

